

VLSI Course Project

Carry Look Ahead Adder

Shaantanu kulkarni

2019102031

Proposed Structure for the Adder

The main goal of building a carry look ahead adder is to minimize the delay as compared to the ripple carry adder where the following adders had to wait for the carry generations from the previous stages.

Consider 2 four-bit numbers that are to be added $a_4a_3a_2a_1$ and $b_4b_3b_2b_1$ and we are generating two signals p_i (propagate signal) and g_i (generate signal).

$$p_i = a_i \oplus b_i$$

$$g_i = a_i.b_i$$

Note: Some notations have been changed from what were given in the question to simplify the interpretability. However the overall circuit is the same.

And the carry bit from i th adder is c_i and sum is sum_i which is given as:

$$c_i = (p_i . c_{(i-1)}) + g_i \text{ where } i = 1,2,3,4.$$


$$sum_i = p_i \oplus c_i$$

- $C_1 = C_0.P_0 + G_0$.
- $C_2 = C_1.P_1 + G_1 = (C_0.P_0 + G_0).P_1 + G_1 = C_0.P_0.P_1 + G_0.P_1 + G_1$
- $C_3 = C_2.P_2 + G_2 = C_1.P_1.P_2 + G_1.P_2 + G_2 = C_0.P_0.P_1.P_2 + G_0.P_1.P_2 + G_1.P_2 + G_2$
- $C_4 = C_3.P_3 + G_3 = C_0.P_0.P_1.P_2.P_3 + P_3.P_2.P_1.G_0 + P_3.P_2.G_1 + G_2.P_3 + G_3$

Some Specifications :

- We know that the C_0 bit is always '0' so we can eliminate the first term in every expression of C_i
- Instead of using multiple input gates, we can use 2 input gates multiple times and reuse the common terms from previous stages so that we reduce the overall number of gates. Specifically, for some three terms and in previous stage can be directly used as input to 2 input and gate which can effectively act as a four input and gate.
- Example: Consider the term $G_0.P_1.P_2$ used to calculate C_3 . Now this term is partially present in $P_3.P_2.P_1.G_0$ which is used to calculate C_4 . This former output can be used to calculate latter directly by anding it with P_3 . Also we are not waiting for any input to set then calculate some value, so its now like ripple adder. We are just reusing some block from previous stage.


Gate Level Diagram of Proposed Adder

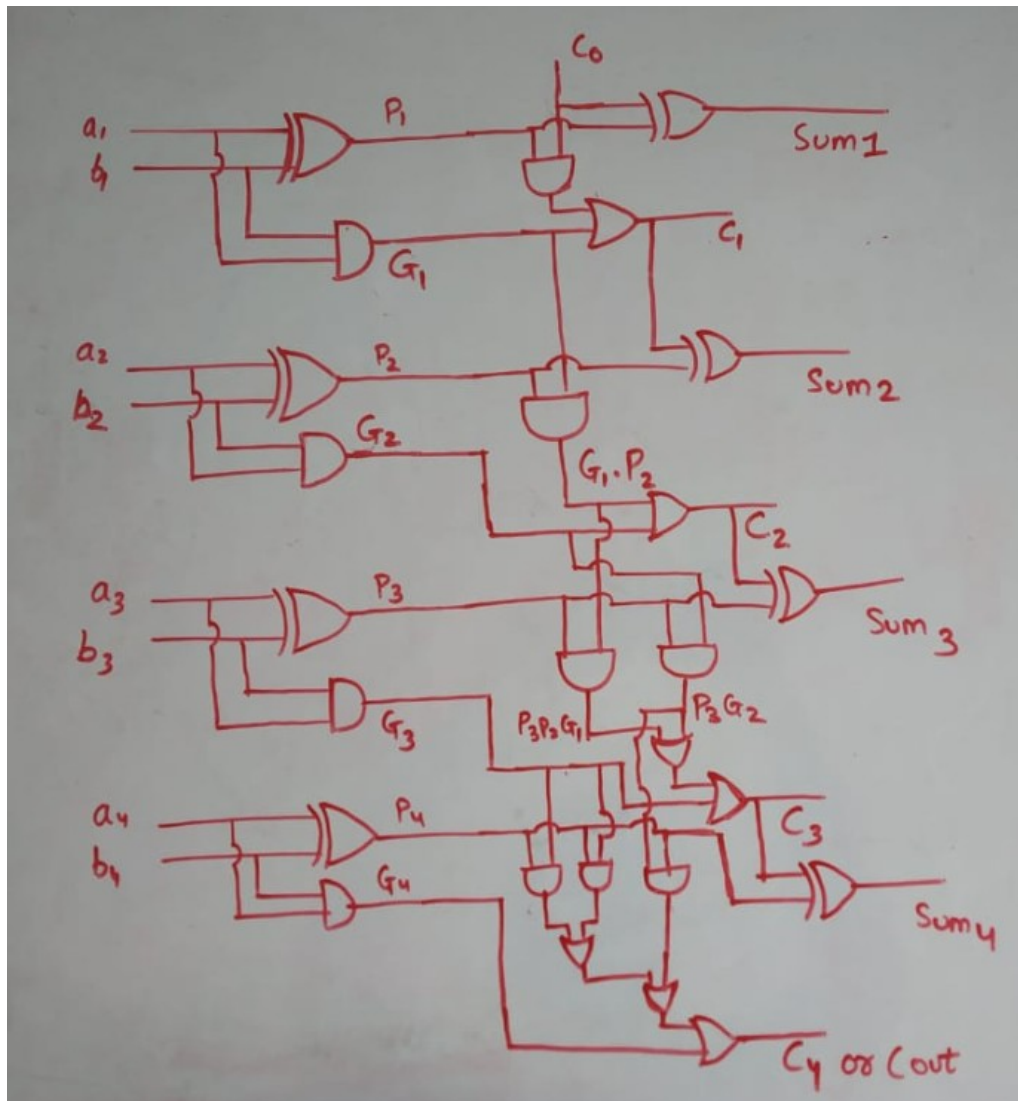

- We can see that C_0 is always zero so we don't need it in later stages
- Reusing the outputs from previous stages reduces number of gates and we don't have to wait like ripple carry adder.


Topology And Sizing

D Flip-Flop

 

The above circuit was used to make D-FlipFlops using pass transistor logic.

Pass Transistor Gate:

 


Dimensions of Pass Transistor :

Pmos width = 20λ

Nmos width = 10λ

D FlipFlop Dimensions:

 

Dimensions of D Flip-Flop :

$18,99\text{ um} \times 11,97\text{ um}$


$= 227.3103\text{ um}^2$

$\sim 28063\lambda^2$

each Pmos has width of 20λ

each Nmos has width of 10λ

Adder Module:

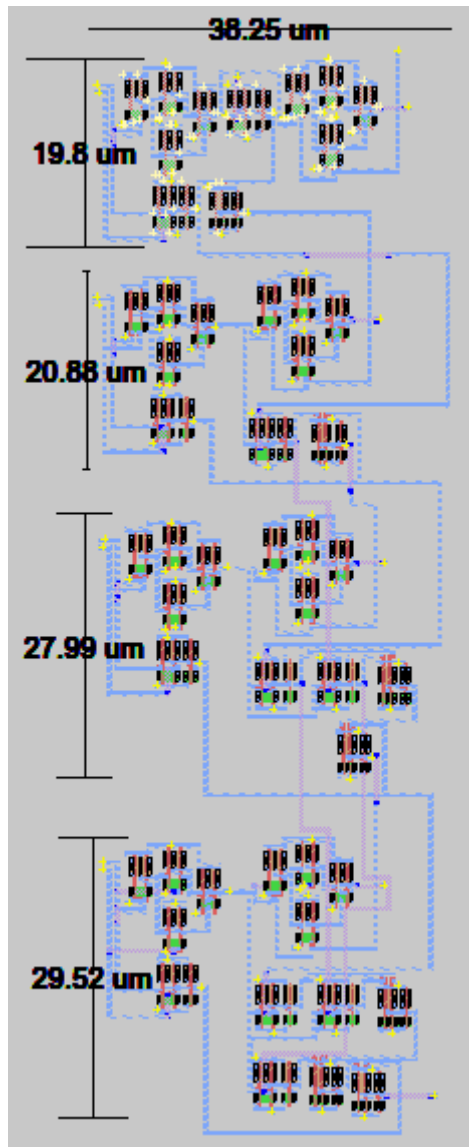

Width of the total Adder circuit:

$$W = 38.25 \text{ um}$$

Heights of individual bit adders:

Adder 1: 19.8um

Adder 2: 20.88um

Adder 3: 27.99um

Adder 4: 29.52um

Total height = 98.19 um

Total chip area covered by Adder:

$$= 38.25\text{um} \times 98.19\text{um}$$

$$= 3755.7675 \text{ um}^2$$

$$\sim 463675 \lambda^2$$

Verification Of Functionality

1) D FlipFlop Functionality

Pass transistor gate Subcircuit:

```
*-----SUBCKT Pass transistor-----
.subckt passgate y d s sb vdd_ gnd_
.param width_N={Width}
.param width_P={2*Width}

*-----PULL up network -----//
M1 y s d vdd_ CMOSP W={width_P} L={2*LAMBDA}
+ AS={5*width_P*LAMBDA} PS={10*LAMBDA+2*width_P} AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

M2 y sb d gnd_ CMOSN W={width_N} L={2*LAMBDA}
+ AS={5*width_N*LAMBDA} PS={10*LAMBDA+2*width_N} AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}


.ends passgate
```

DFF Subcircuit using two D latches in master slave arrangement:

```
*----- SUBCKT D FLIP FLOP -----
.subckt DFF Q_ D_clk_clkb_ vdd_ gnd_
x2 in1 D_clk_clkb_ vdd_ gnd_ passgate
x3 in2 in1 clkb_ clk_ vdd_ gnd_ passgate
x4 out1_ in1 vdd_ gnd_ inv
x5 in2 out1_ vdd_ gnd_ inv

x6 out1_ in3 clkb_ clk_ vdd_ gnd_ passgate
x7 in4 in3 clk_ clkb_ vdd_ gnd_ passgate
x8 Q_ in3 vdd_ gnd_ inv
x9 in4 Q_ vdd_ gnd_ inv
.ends DFF
```

Simulation Results:

 

- The Topmost signal is the input signal to the D FlipFlop
- Middle one is the output from the D FlipFlop
- The lower plot shows the clock signal
- Clk Timeperiod = 10ns

1) CLA module Functionality

CLA module netlist

```
Vc0 c0 gnd 0V

xp1 p1 a1 b1 vdd gnd xor
xp2 p2 a2 b2 vdd gnd xor
xp3 p3 a3 b3 vdd gnd xor
xp4 p4 a4 b4 vdd gnd xor

xg1 g1 a1 b1 vdd gnd and
xg2 g2 a2 b2 vdd gnd and
xg3 g3 a3 b3 vdd gnd and
xg4 g4 a4 b4 vdd gnd and

xp1c0 p1c0 p1 c0 vdd gnd and
xp2g1 p2g1 p2 g1 vdd gnd and
xp3g2 p3g2 p3 g2 vdd gnd and
xp3p2g1 p3p2g1 p3 p2g1 vdd gnd and
xp4p3p2g1 p4p3p2g1 p4 p3p2g1 vdd gnd and
xp4p3g2 p4p3g2 p4 p3g2 vdd gnd and
xp4g3 p4g3 p4 g3 vdd gnd and

// intermediate nodes
x31 i31 p3p2g1 p3g2 vdd gnd or
x41 i41 p4p3p2g1 p4p3g2 vdd gnd or
x42 i42 i41 p4g3 vdd gnd or

xc1 c1 p1c0 g1 vdd gnd or
xc2 c2 p2g1 g2 vdd gnd or
xc3 c3 i31 g3 vdd gnd or
xc4 c4 i42 g4 vdd gnd or

xsum1 sum1 p1 c0 vdd gnd xor
xsum2 sum2 p2 c1 vdd gnd xor
xsum3 sum3 p3 c2 vdd gnd xor
xsum4 sum4 p4 c3 vdd gnd xor
```

Total number of gates used:

XOR : 8 gates

AND : 11 gates

OR : 7 gates

Total gates used: 25 gates:


For testing the functionality two testcases are used:

- input A = 0101 ; input B = 1000
- input A = 0110 ; input B = 0011





Input A







Input B

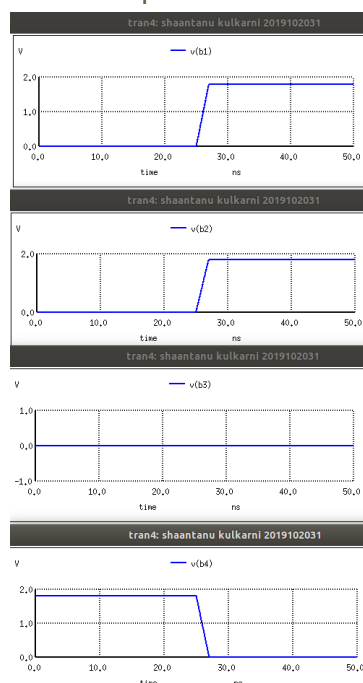

Sum bits:

    






Carry bits:

    


As expected the outputs of the two testcases are

- sum = 1101 & c1 = 0, c2=0, c3= 0, c4=0
- sum = 1001 & c1=0, c2=1, c3=1, c4=0

Stick diagrams of unique gates

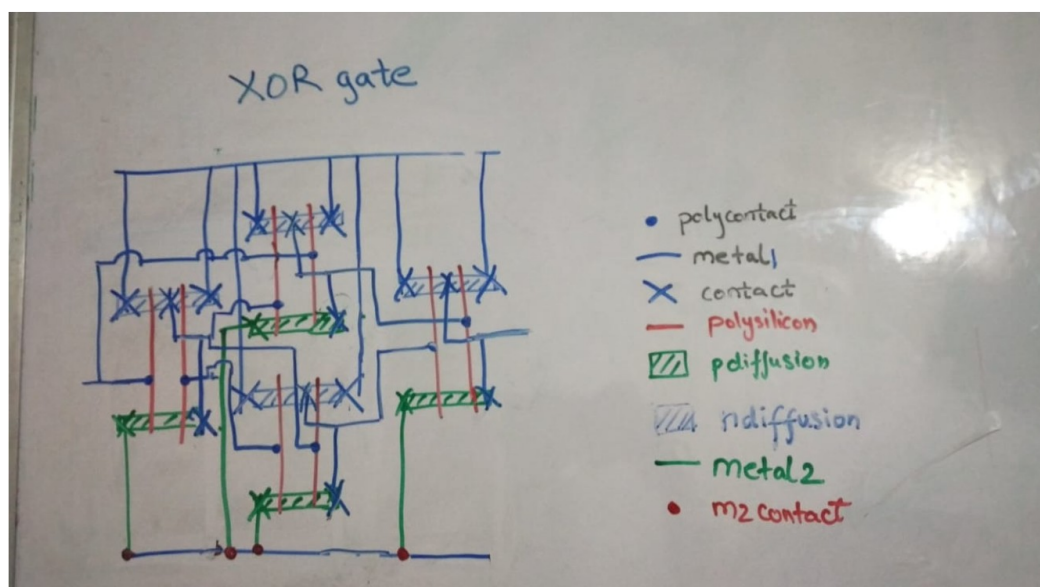  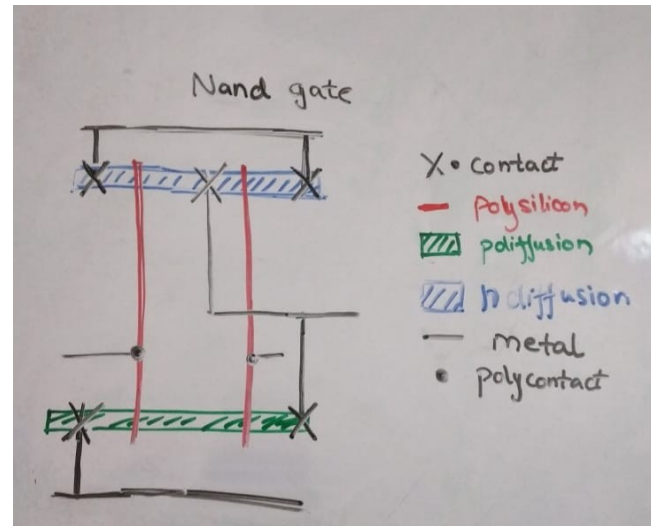 

D Flip Flop Delays

 

Delays:

$$T_{dhl} = 0.11\text{ns} \quad T_{dhl} = 0.33\text{ns}$$

$$T_{pd} = (T_{dhl} + t_{dlh})/2 = (0.33 + 0.11)/2 = 0.22 \text{ ns}$$

For T-setup, the rise time of the input is increased slowly unless we can see distorted outputs. It was found that

$$T_{\text{setup}} = 0.044\text{ns}$$


For T-hold, after the input was reflected at output of Dff, the input was suddenly changed and this time interval was decreased until distorted output was seen.

$$T_{\text{hold}} = 0.05\text{ns}$$


Layouts

Note: For simulation of all the gates , all possible 4 inputs are provided and the output is check


OR gate:

 


tran1: shaantanu kulkarni 2019102031

 


tran1: shaantanu kulkarni 2019102031

 



tran1: shaantanu kulkarni 2019102031

 


AND gate:

 




Results:

  


NAND gate:

 




Results:

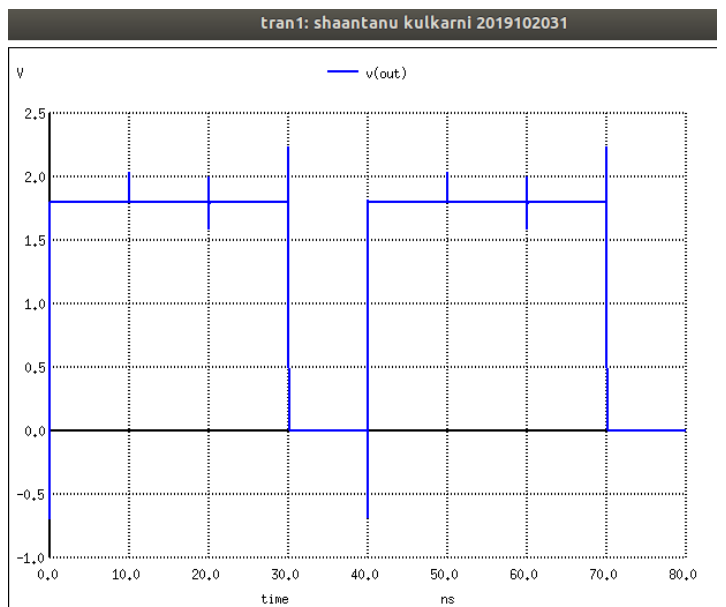  


XOR gate:

 

Results:

  
 



D FlipFlop:

 

Results:

  - The red plot is Clock signal and blue is the input to D flipflop
- The signal Q is the output of D flipflop which is updated at positive edge of the clock signal



 

Delays:

$$T_{dhl} = 0.13\text{ns} \quad T_{dlh} = 0.089\text{ns}$$

$$T_{pd} = (T_{dhl} + t_{dlh})/2 = (0.13 + 0.089)/2 = 0.1095 \text{ ns}$$


For T-setup, the rise time of the input is increased slowly unless we can see distorted outputs. It was found that

$$T_{\text{setup}} = 0.038\text{ns}$$

For T-hold, after the input was reflected at output of Dff, the input was suddenly changed and this time interval was decreased until distorted output was seen.

$$T_{\text{hold}} = 0.035\text{ns}$$

CLA module:

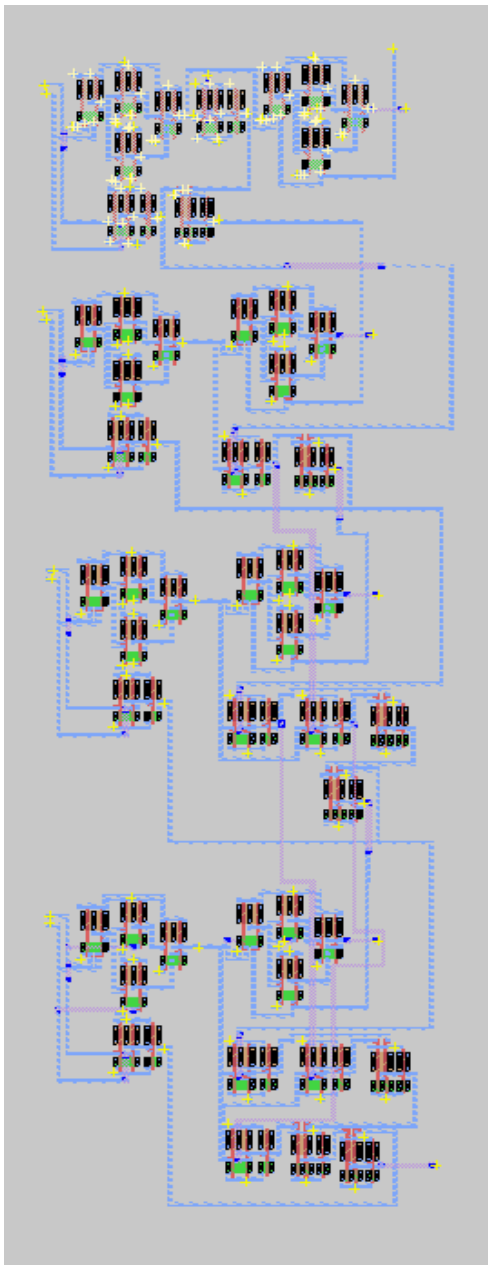


For testing the functionality two testcases are used:


- input A = 0101 ; input B = 1000
 - input A = 0110 ; input B = 0011

Input A

Input B

 


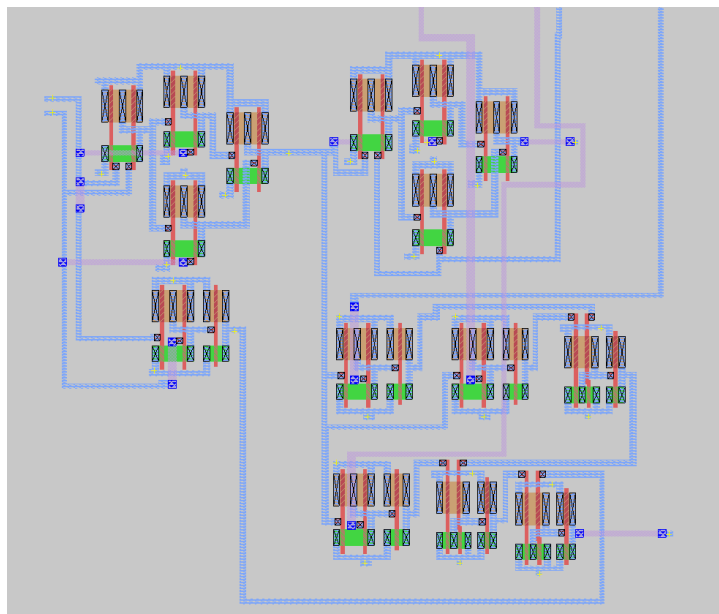A screen shot of last bit adder to show the layout clearly




Results of post layout CLA module

Sum Bits:

 

Carry bits:

 

As expected the outputs of the two testcases are

- sum = 1101 & c1 = 0, c2 = 0, c3 = 0, c4 = 0
- sum = 1001 & c1 = 0, c2 = 1, c3 = 1, c4 = 0

Complete integrated simulation in Ngspice

For testing the complete integrated circuit , the test cases chosen are such that the worst case delay is expected on this test case.



Testcase:

We want a testcase such that all the sum bits are changed and most of the voltages at the internal nodes change .



Say that the initial values of inputs are both (0000)₂ so , the sum will also be (0000)₂. Now we want the sum to change to (1111)₂ and we also want maximum intermediate node values to change so that the delay is maximized.

It turns out that if we choose input like A= (1010) and B = (0101), the sum will be (1111) and most of the intermediate tends to change . The intuition is that since $A_i \neq B_i$ for i th bit, there are many xor gates in circuit. Initially these are at '0'. Now in the next clock cycle all these xors will change. Xor gates will have maximum delay because of 4 internal nand gates used in it.

Inputs:

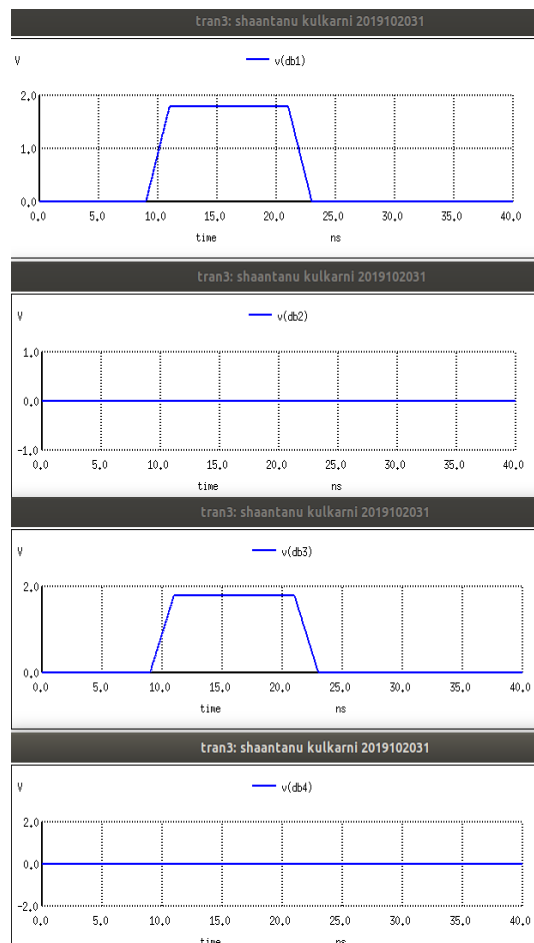 


D flipflops (Inputs)

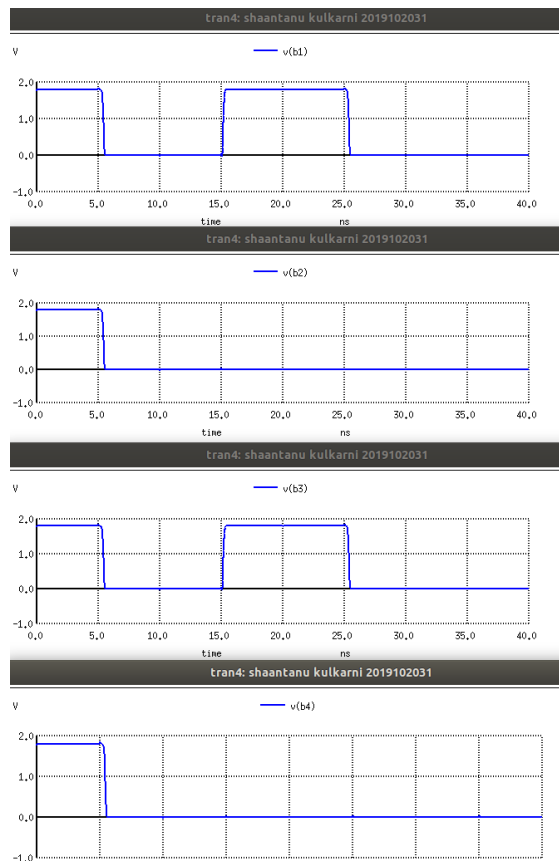 


Note: The initially '1' values are garbage initial values at the output of D flipflop. This are set to correct values after the first positive edge of clock at 5ns.

Note: Blue plot is the sum output and qi (red plot) is output of final D flipflop which is updated after one clock cycle as expected. So , initially for one and half clock cycle the output of D flipflop is corrupted.


Sumbit 1 (LSB)

 


Sumbit 2

 

Sumbit 3

 


Sumbit4 (MSB)

 

Cout

tran6: shaantanu kulkarni 2019102031

 

Delays:

Sum bit	Tlh (ns)	Thl (ns)
S1	0.4164	0.4186
s2	0.4070	0.4352
s3	0.4375	0.4455
s4	0.4375	0.4776


Thus the worst case delay is Thl for s4 ie 0.4776 ns . Thus maximum delay taken by any input , for the sum to be calculated is about 0.4776ns.

Maximum clock frequency = 1/minimum time period

$$= 1/(\text{delay of Dff} + \text{worst delay of CLA} + \text{hold time})$$


$$= 1/(0.44+0.4776+0.05) = 1.03348 \times 10^9 \text{ Hz}$$

Floor Plan

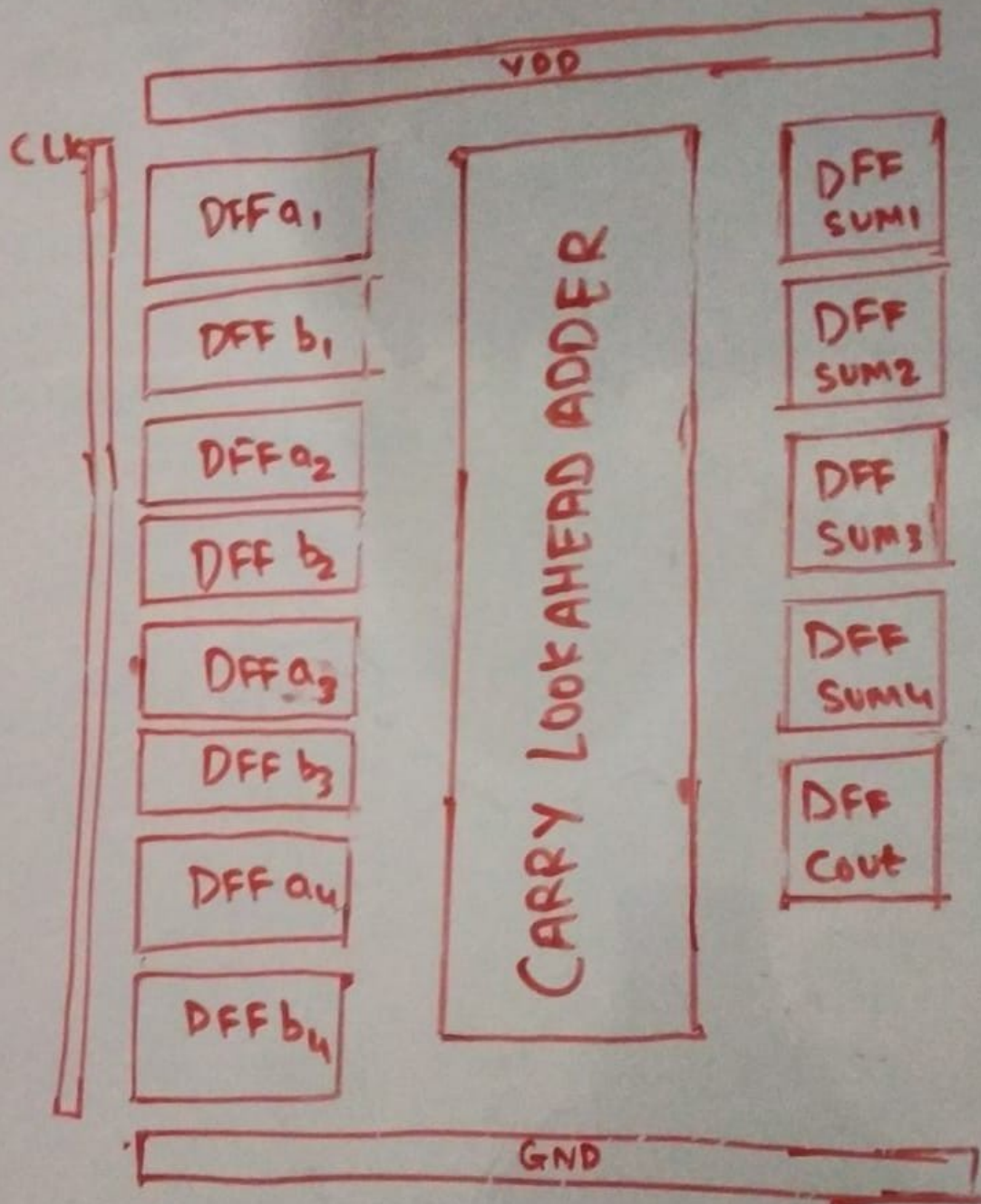


FLOOR PLAN OF COMPLETE CIRCUIT

Complete Layout

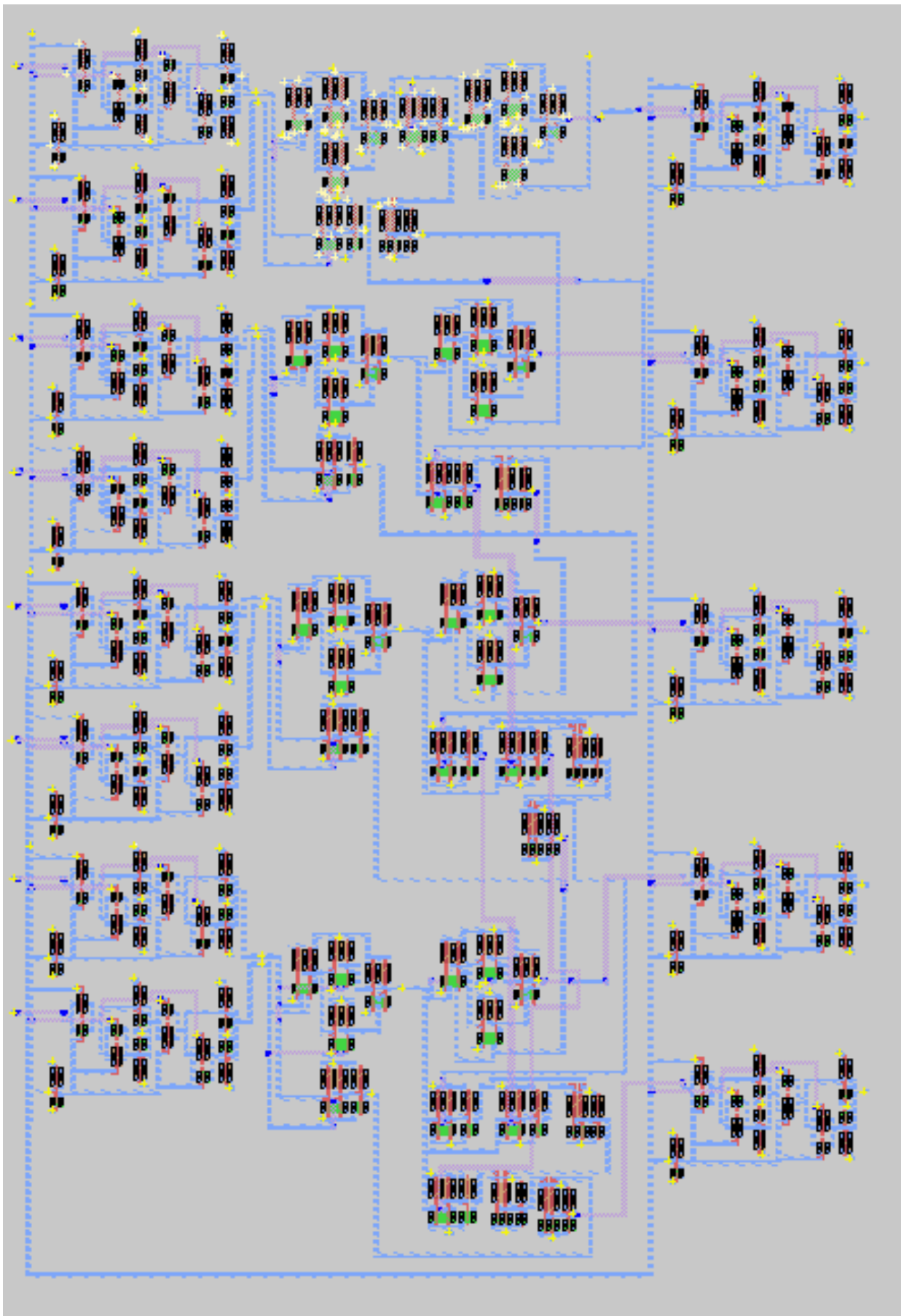

Some other screenshots of the complete layout

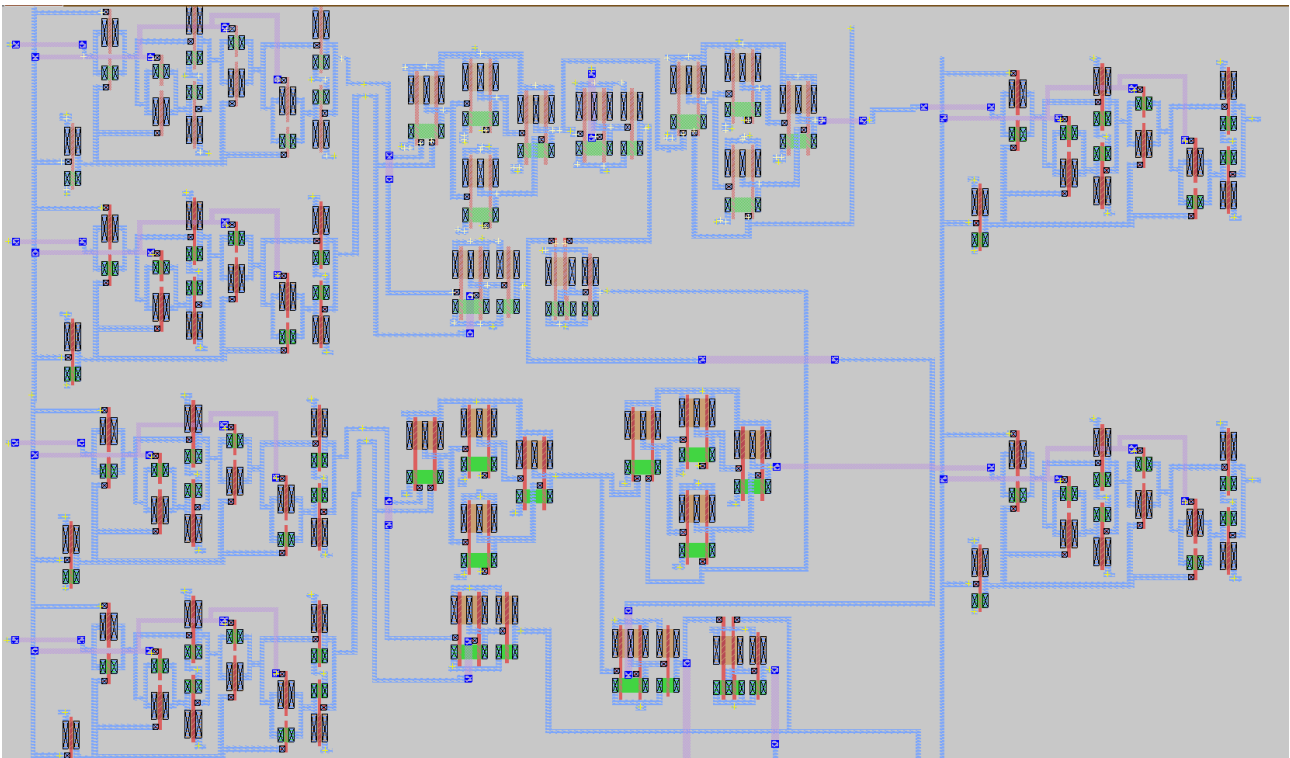Zoomed in view of the layout for the first two bits. Here we can see 4 D flipflops on the left hand side and 2 D flipflops on the right hand sideZ











Simulation specific note:


As explained in previous part about the choice of input test cases, for the simulation of this part also we have taken the same test cases.

Simulations and Results:


Inputs:

        


Sumbit1 (LSB)

 

Sumbit2

 


Sumbit3

 

Sumbit4 (MSB)

tran3: shaantanu kulkarni 2019102031

 

Delays:

Sum bit	Tlh (ns)	Thl (ns)
S1	0.4478	0.5219
s2	0.4627	0.5319
s3	0.4861	0.5597
s4	0.5320	0.5670

Thus the worst case delay is Thl for s4 ie 0.567 ns . Thus maximum delay taken by any input , for the sum to be calculated is about 0.567ns.


Maximum clock frequency = minimum time period

= delay of Dff + worst delay of CLA + hold time

= 0.1095+0.567+0.035 = 1.4054 x 10⁹ Hz

Verilog Simulations:

Inputs

 

Output sums and output of flipflops:



- We can see that the outputs of flipflops are set after one clock cycle delay as expected
- The positive edge behavior of the D flipflop can be seen clearly
- The outputs of sum are as expected which supports the fact that the functionality of the circuit is correct.

Verilog Structural description

```
module CarryLA_4(a,b,ci,sum,co);

input [3:0] a,b;
input ci;

output [3:0] sum;
output co;

wire[3:0] g,p,cout;
wire G0,P0;
wire[9:0] w;

// Calculation of Propagate signal Pi
xor x0(prop[0],a[0],b[0]);
xor x1(prop[1],a[1],b[1]);
xor x2(prop[2],a[2],b[2]);
xor x3(prop[3],a[3],b[3]);

// Calculation of Generate signal Gi
and a0(gen[0],a[0],b[0]);
and a1(gen[1],a[1],b[1]);
and a2(gen[2],a[2],b[2]);
and a3(gen[3],a[3],b[3]);

and and0(w[0],prop[0],ci);
or or0(cout[0],gen[0],w[0]);

and and1(w[1],prop[1],prop[0],ci);
and and2(w[2],prop[1],gen[0]);
or or1(cout[1],gen[1],w[2],w[1]);

and and3(w[3],prop[2],prop[1],prop[0],ci);
and and4(w[4],prop[2],prop[1],gen[0]);
and and5(w[5],prop[2],gen[1]);
or or2(cout[2],gen[2],w[5],w[4],w[3]);

and and6(w[6],prop[3],prop[2],prop[1],gen[0]);
and and7(w[7],prop[3],prop[2],gen[1]);
and and8(w[8],prop[3],prop[2],prop[1],prop[0],ci);
and and9(w[9],prop[3],gen[2]);
or or3(cout[3],gen[3],w[9],w[8],w[7],w[6]);

and and10(co,cout[3],1);

// Calculation of Sum bits
xor xor0(sum[0],prop[0],ci);
xor xor1(sum[1],prop[1],cout[0]);
xor xor2(sum[2],prop[2],cout[1]);
xor xor3(sum[3],prop[3],cout[2]);

endmodule
```